


Sequential Circuits



Index


- Sequential Logic
- Bistable element
- Latches
 - SR Latch
 - D Latch
- Flip-Flops
 - D Flip-Flop
 - Register
 - Enabled Flip-Flop
 - Resettable Flip-Flop
- Transistor-Level Design
- Problematic circuits
 - Astable circuits
 - Race Condition
 - Asynchronous circuits
- Synchronous circuits

Sequential Logic

- The output of **combinational logic** depends only on **current input** values
 - given a specification in the form of a truth table or boolean equation, we can create an optimized circuit to meet the specification
- The outputs of **sequential logic** depend on both **current and prior input** values
 - has **memory**
 - explicitly remember previous inputs
 - or it might **distil the prior inputs into a smaller amount of information** called the **state of the system**
 - a set of bits (**state variables**) that contain all the information about the past necessary to explain the future behaviour of the circuit
 - **latches** and **flip-flops** are simple sequential circuits that store **one bit of state**
- Sequential circuits are **complicated to analyse**
 - we can discipline ourselves to build only **synchronous** sequential circuits
 - combinational logic and banks of flip-flops containing the state of the circuit

Bistable element (1)

- The fundamental building block of **memory**: an element **with two stable states**
 - The inverters are cross-coupled
 - the input of I1 is the output of I2 and vice versa
 - the circuit has no inputs, but it does have two outputs
- This circuit is **cyclic**
 - Case 1: $Q = 0$
 - I2 receives a FALSE input, so it produces a TRUE output on \bar{Q}
 - I1 receives a TRUE input, so it produces a FALSE output on Q
 - this is consistent with the original assumption ($Q = 0$), so it is **stable**
 - Case 2: $Q = 1$
 - I2 receives a TRUE input and produces a FALSE output on \bar{Q}
 - I1 receives a FALSE input and produces a TRUE output on Q
 - this is again stable
- Because the cross-coupled inverters have **two stable states**, the circuit is said to be **bistable**

 


Bistable element (2)

- An element with N stable states conveys $\log_2 N$ bits of information, so a bistable element stores **one bit**
 - state of the cross-coupled inverters is contained in one binary state variable (Q)
 - the value of Q tells us everything about the past that is necessary to explain the future behaviour of the circuit
 - if $Q=0$, it will remain 0 forever
 - if $Q=1$, it will remain 1 forever
- When power is first applied to a sequential circuit, the initial state is **unknown** and usually **unpredictable**
 - it may differ each time the circuit is turned on
- Although the cross-coupled inverters can store a bit of information, they are not practical because the **user has no inputs to control the state**


SR Latch (1)

- Two cross-coupled NOR gates

 

- Like the cross-coupled inverters, but its **state can be controlled** through the inputs
 - set (S) and reset (R) the output
- Case 1: $R=1, S=0$
 - N1 sees at least one TRUE input R, so it produces a FALSE output on Q
 - N2 sees both Q and S FALSE, so it produces a TRUE output on \bar{Q}
- Case 2: $R=0, S=1$
 - N1 receives inputs of 0 and \bar{Q} , however we don't yet know \bar{Q}
 - N2 receives at least one TRUE input S, so it produces a FALSE output on \bar{Q}
 - Now we can revisit N1, so the output Q is TRUE

SR Latch (2)

 

- Case 3: $R=1, S=1$
 - N1 and N2 both see at least one TRUE input, so each produces a FALSE output
- Case 4: $R=0, S=0$
 - N1 receives inputs of 0 and \bar{Q} , however we don't yet know \bar{Q}
 - N2 receives inputs of 0 and Q . however we don't yet know Q
 - now we are stuck, but we know that Q must either be 0 or 1
 - Case 4a: $Q=0$
 - N2 produces a TRUE output on \bar{Q}
 - N1 receives one TRUE input (\bar{Q}), so its output is FALSE, just as we had assumed
 - Case 4b: $Q=1$
 - N2 produces a FALSE output on \bar{Q}
 - N1 receives two FALSE inputs, so its output is TRUE, just as we had assumed
 - Putting this all together: when R and S are 0, Q will **remember** the old value
 - this circuit has **memory**

SR Latch (3)

- The truth table summarizes these four cases



- The inputs S and R stand for **Set** and **Reset**
 - “set” a bit means to make it TRUE
 - “reset” a bit means to make it FALSE
- When neither input is asserted, Q **remembers** its old value
- Asserting both S and R simultaneously **doesn't make sense**
 - it means the latch should be set and reset at the same time
 - the confused circuit responds by making both outputs 0


SR Latch VHDL

```
entity SR_LATCH is
  port( S: in std_logic;
        R: in std_logic;
        Q: out std_logic
  );
end SR_LATCH;
```


```
architecture rtl of SR_LATCH is
begin
  latch: process(S, R)
  begin
    if( S='1' and R='0') then
      Q <= '1';
    elsif( S='0' and R='1') then
      Q <= '0';
    elsif( S='0' and R='0') then
      null;
    elsif( S='1' and R='1') then
      Q <= 'X';
    end if;
  end process;
end rtl;
```

D Latch

- SR latch is awkward
 - it behaves strangely when both S and R are simultaneously asserted
 - moreover, S and R conflate the **issues of what and when**
 - asserting one input determines **what** the state should be and **when** it should change
- Design is easier when these questions (what and when) are **separated**
- The D latch avoids the strange case of simultaneously asserted R and S inputs
 - **data input** D controls what the next state should be
 - **clock input** CLK controls when the state should change
 - if CLK=0, S and R are FALSE (regardless of D) and Q remembers its old value
 - if CLK=1, one AND is TRUE and the other is FALSE (depending on D) and Q = D
 - In all cases, \bar{Q} is the complement of Q

 

CLK	D	S	R	Q	\bar{Q}
0	x	0	0	Q_{prev}	\bar{Q}_{prev}
1	0	0	1	0	1
1	1	1	0	1	0

 

D Latch VHDL

```
entity D_LATCH is
    port( D: in std_logic;
          CLK: in std_logic;
          Q: out std_logic
    );
end D_LATCH;
```


```
architecture rtl of D_LATCH is
    begin
        latch: process(D, CLK)
        begin
            if( CLK = '1' ) then
                Q <= D;
            end if;
        end process;
    end rtl;
```

Clock

- The clock controls **when** data flows through the latch
 - when $CLK = 1$, the latch is **transparent**
 - data at D flows through to Q as if the latch were just a buffer
 - when $CLK = 0$, the latch is **opaque**
 - it blocks the new data from flowing through to Q, and Q retains the old value

D Flip-Flop

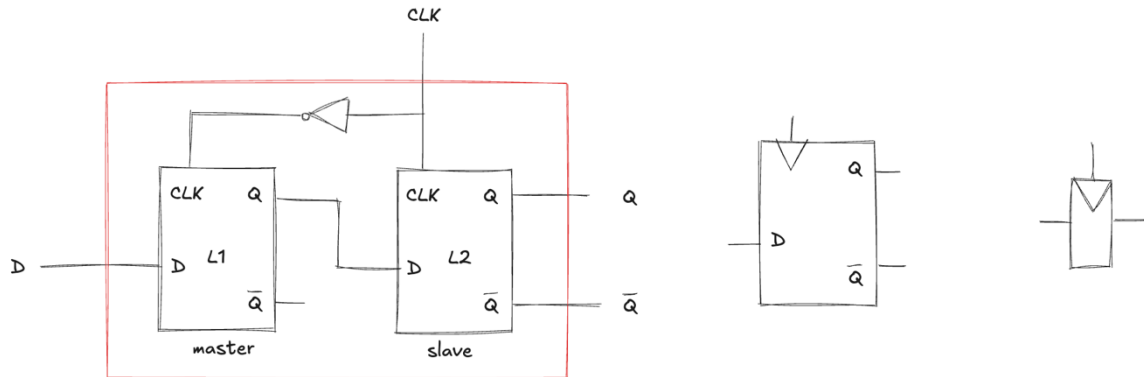- Two back-to-back D latches controlled by complementary clocks




- L1 is called the **leader/master**
 - L2 is called the **follower/slave**
- It copies D to Q on the **rising edge** of the clock and remembers its state at all other times:
 - when CLK=0, the master is transparent and the slave is opaque
 - when CLK=1, the master goes opaque and the slave becomes transparent
- The **D input** specifies **what** the new state will be, the **clock edge** indicates **when** the state should be updated

D Flip-Flop VHDL

```
entity D_FF is
    port( CLK: in std_logic;
          D: in std_logic;
          Q: out std_logic
        );
end D_FF;
```


```
architecture rtl_rising_edge of D_FF is
... begin
... ff: process(CLK)
... begin
... if(CLK'event and CLK='1') then
...     Q <= D;
... end if;
... end process;
end rtl_rising_edge;
```

```
state_register : process(CLK)
begin
    if rising_edge(CLK) then
        Q <= Q_next;
    end if;
end process;
```



Flip-Flop and Latch comparison


 
- Apply D and CLK inputs to a D latch and a D flip-flop to determine Q



- The initial value of Q is **unknown**
- Consider the latch:
 - on the first CLK rising edge, D=0 so Q becomes 0
 - each time D changes while CLK=1, Q follows
 - when D changes while CLK=0, D is ignored
- Consider the flip-flop:
 - **on each CLK rising edge**, D is copied to Q
 - at all other times, Q retains its state

Register

  - An N-bit register is a **bank** of N flip-flops that **share a common CLK**
 - all bits of the register are updated at the same time
 - registers are the **key building block of most sequential circuits**



Register VHDL



```
entity Register is
  generic(N : integer := 8);
  port(CLK : in  std_logic;
       D   : in  std_logic_vector(N-1 downto 0);
       Q   : out std_logic_vector(N-1 downto 0)
  );
end Register;
```

```
architecture structural of Register is
  component D_FF is
    port(CLK : in  std_logic;
         D   : in  std_logic;
         Q   : out std_logic
    );
  end component;
begin
  GEN_FF : for i in 0 to N-1 generate
    FF_i : D_FF
      port map(CLK => CLK, D => D(i), Q => Q(i));
  end generate GEN_FF;

end structural;
```

Enabled Flip-Flop

- Another input called **Enable** to determine if data is loaded on the clock edge
 - when Enable is TRUE, the flip-flop behaves like an ordinary D flip-flop
 - when Enable is FALSE, the flip-flop ignores the clock and retains its state
- Useful when we wish **to load a new value into a flip-flop only some of the time**, rather than on every clock edge
- Two ways to implement it
 - an input multiplexer:
 - the value D pass if Enable is TRUE
 - the old state is recycled if Enable is FALSE
 - the clock can be gated:
 - if Enable is TRUE, the CLK toggles normally
 - if Enable is FALSE, the CLK input is also FALSE
 - notice that Enable must not change while CLK=1 or the flip-flop see a **clock glitch** (switch at an incorrect time)
- Generally, **performing logic on the clock is a bad idea**

  


Enabled Flip-Flop VHDL

```
entity DFF_en is
    port(CLK : in  std_logic;
          EN  : in  std_logic;
          D   : in  std_logic;
          Q   : out std_logic
    );
end entity;
```

```
architecture rtl of DFF_en is
begin
    process(CLK)
    begin
        if rising_edge(CLK) then
            if EN='1' then
                Q <= D;
            end if;
        end if;
    end process;
end rtl;
```

Resettable Flip-Flop

 - Another input, called **Reset**
 - when Reset is FALSE, the flip-flop behaves like an ordinary D flip-flop
 - when Reset is TRUE, the flip-flop ignores D and resets the output to 0
- Useful when we want to **force a known state into all the flip-flops** in a system when we first turn it on
- We can construct it from an ordinary D flip-flop and an AND gate



- the reset is an **active low signal**, meaning that it performs its function when it is 0
- by adding an inverter, the circuit could have accepted an **active high** reset signal

Resettable Flip-Flop


```
entity DFF_reset_low is
  port(CLK    : in  std_logic;
        RESET : in  std_logic;  -- active low
        D      : in  std_logic;
        Q      : out std_logic
  );
end entity DFF_reset_low;
```

```
architecture rtl of DFF_reset_low is
  signal D_int : std_logic;
begin
  -- Active-low reset implemented via AND gate
  D_int <= D and RESET;

  process(CLK)
  begin
    if rising_edge(CLK) then
      Q <= D_int;
    end if;
  end process;
end architecture rtl;
```


Transistor-Level Design (1)

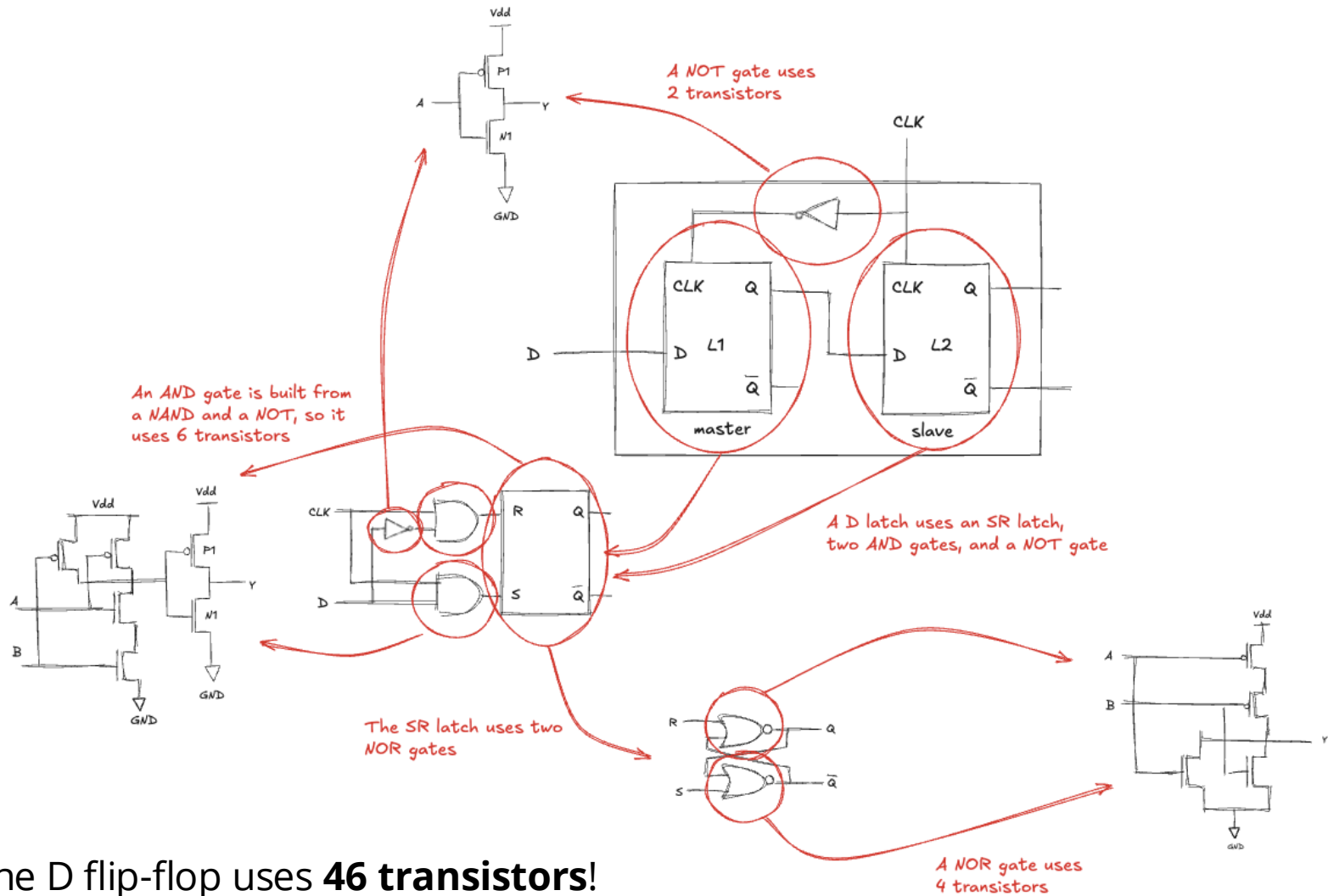- How many transistors are needed to build the D flip-flop?




Transistor-Level Design (2)

- Many transistors when built from logic gates!
- Its fundamental role is to be **transparent or opaque**, much **like a switch**
- A compact D latch can be constructed from **a single transmission gate**
 - when $CLK=1$, the transmission gate is ON, so D flows to Q and the latch is transparent
 - when $CLK=0$, the transmission gate is OFF, so Q is isolated from D and the latch is opaque
- Two major limitations:
 - **floating node**: when the latch is opaque, Q is not held at its value by any gates, after some time, noise and charge leakage may disturb the value of Q
 - **no buffers**
 - a spike of noise that pulls D to a negative voltage can turn on the nMOS transistor, making the latch transparent, even when $CLK=0$;
 - likewise, a spike on D above VDD can turn on the pMOS transistor even when $CLK=0$
 - neither the input of a transmission gate nor the state node of a sequential circuit **should ever be exposed to the outside world** where noise is likely

 


Transistor-Level Design (3)

 - A more robust (12-transistor) D latch used on modern commercial chips
 - still built around a clocked transmission gate
 - adds inverters to buffer the input and output
 - however, it is outside the scope of this course...





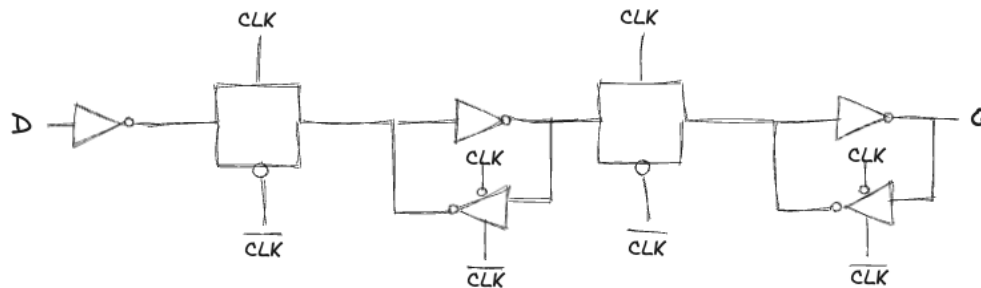- So, a D flip-flop requires only 20 transistors:



  
Problematic circuit: astable circuits

- Consider the three inverters tied in a loop
 - each inverter has a delay of 1ns
- Suppose X is initially 0, then $Y=1$, $Z=0$, and, hence, $X=1$
 - which is inconsistent with original assumption
 - the circuit has **no stable states** and is said to be **unstable** or **astable**
- The period of the oscillator depends on the propagation delay
 - if X rises at $t=0$, Y falls at 1ns, Z rises at 2ns, and X falls at 3ns
 - in turn, Y rises at 4ns, Z falls at 5ns, and X rises again at 6ns
 - then, the pattern will repeat: each node oscillates with a period of 6 ns
 - this circuit is called a **ring oscillator**
- The gate delay depends on how the inverter supply voltage, and even the temperature
 - the ring oscillator period is difficult to accurately predict



 Problematic circuit: race condition (1)

- Consider the following circuits, it seems a good implementation of a D latch (it use fewer gates):






$$= CLK D + CLK Q_{prev}$$

CLK	D	Q_{prev}	Q
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

- The circuit has a **race condition** that causes it to fail when certain gates are slower than others:
 - suppose that $CLK=D=1$, the latch is transparent and passes D through to make $Q=1$
 - now, CLK falls, the latch should remember its old value, keeping $Q=1$
 - however, if the **delay** through the inverter is longer than delays of AND and OR
 - N1 and Q may both fall before CLK rises
 - N2 will never rise, and Q becomes stuck at 0

Problematic circuit: race condition (2)

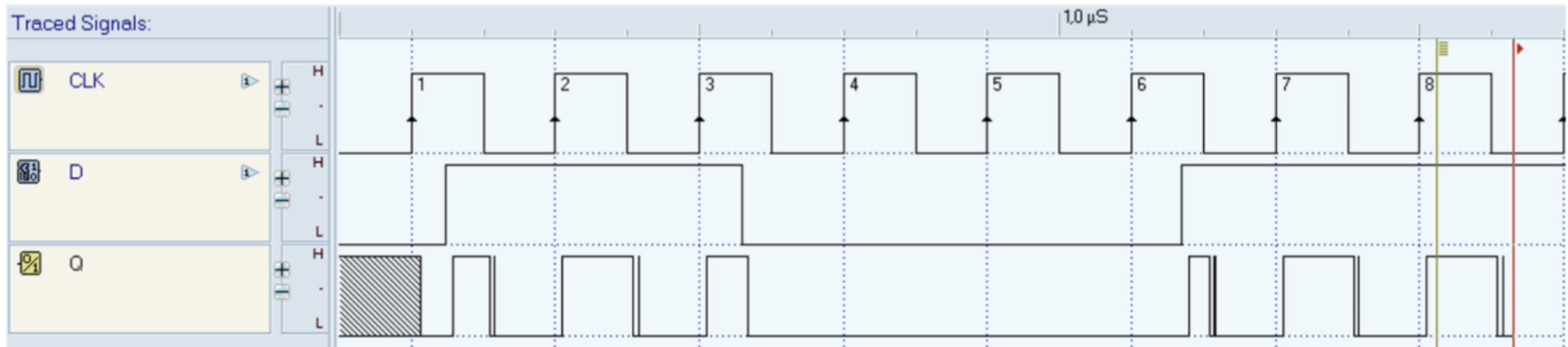 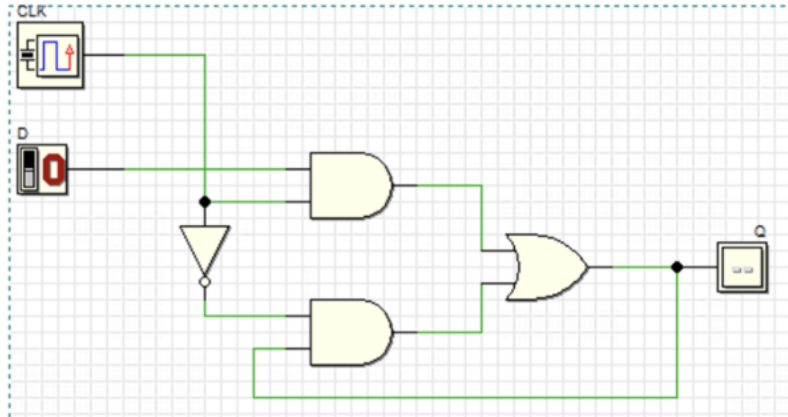


Problematic circuit: asynchronous circuits

- The previous examples contain **loops** called **cyclic paths**
 - outputs are directly fed back to inputs
- The behaviour depends on which of the paths through logic gates is fastest
 - **asynchronous circuits**
 - a circuit works, an identical one built of gates with different delays may not work
 - a circuit works only at certain temperatures at which the delays are just right
 - these malfunctions are **extremely difficult to track down**
- We **break the cyclic paths** by **inserting registers**
 - transforms the circuit into a **collection of combinational logic and registers**
 - registers contain the **state of the system**, which **changes only at the clock edge**
 - the state is **synchronized** to the clock
 - if the clock is **sufficiently slow** all **races are eliminated**
 - inputs to all registers settle before the next clock edge


Synchronous circuits (1)

- A **synchronous sequential circuit** has a **clock input**, whose rising edges indicate a sequence of times at which state transitions occur
 - **current state** and **next state** distinguish the state of the system at the present from the state to which it will enter on the next clock edge
- **Rules of synchronous sequential circuit composition**
 - a circuit is a synchronous if it consists of interconnected elements, such that
 - every element is either a register or a combinational circuit
 - at least one circuit element is a register
 - all registers receive the same clock signal
 - every cyclic path contains at least one register
- A flip-flop is the simplest synchronous sequential circuit
 - it has one input, one clock, one output, and two states
 - the next state is D and the output Q is the current state

 


Synchronous circuits (2)

 
- Which of the following circuits are synchronous sequential circuits?




combinational
it has no registers

 


sequential
no feedback

 

 
no combinational, no synchronous
it has a latch that is
neither a register
nor a combinational circuit



synchronous sequential

 


 no combinational, no synchronous
it has a cyclic path
but no register in the path



no synchronous sequential
the second register receives a different clock
signal than the first
delayed by two inverter delays

Synchronous circuits (3)

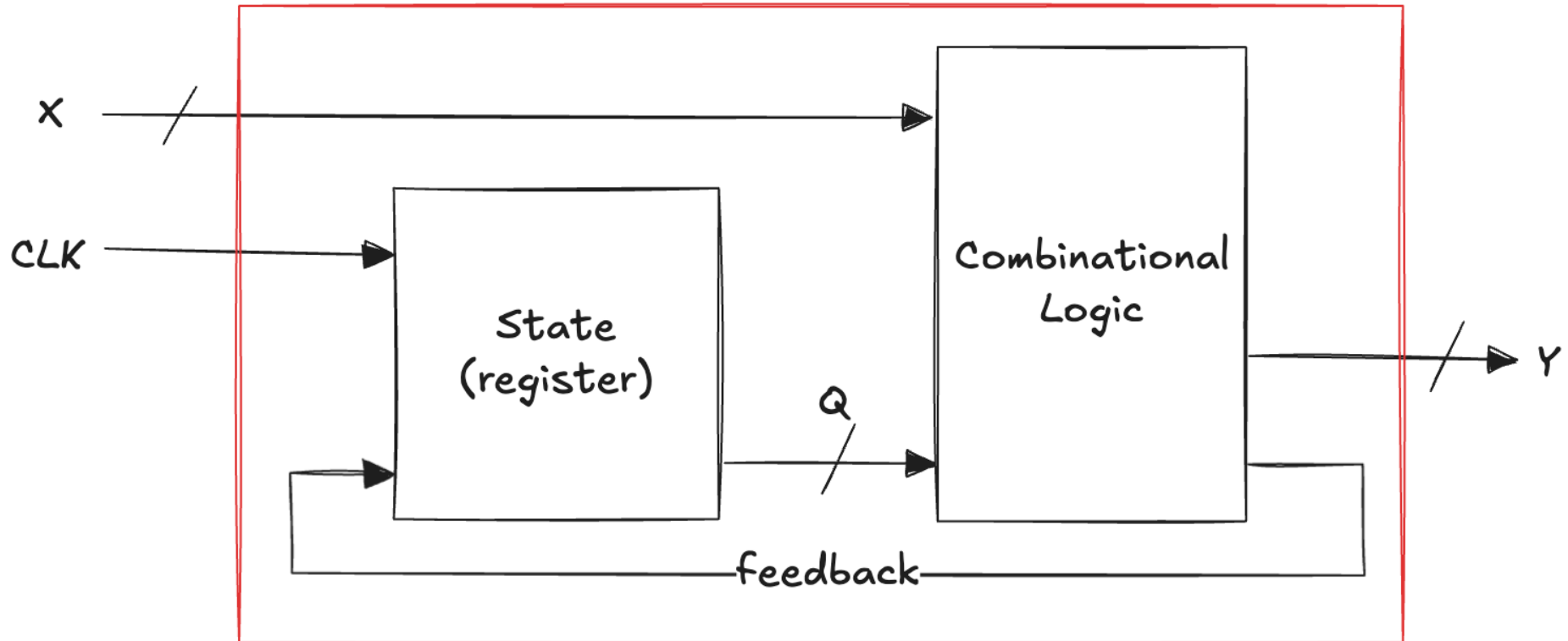

Synchronous circuits VHDL

```
entity SyncCircuit is
    generic(N : integer := 4 -- number of state bits);
    port(CLK : in  std_logic;
         X  : in  std_logic_vector(N-1 downto 0); -- external inputs
         Y  : out std_logic_vector(N-1 downto 0) -- outputs
    );
end SyncCircuit
```

```
architecture Behavioral of SyncCircuit is
```

```
    -- State register
    signal Q      : std_logic_vector(N-1 downto 0); -- current state
    signal Q_next : std_logic_vector(N-1 downto 0); -- next state
```

```
begin
```

```
    -- 1. COMBINATIONAL LOGIC:
```

```
    comb_logic : process(X, Q)
```

```
    begin
```

```
        -- default assignments (mandatory for combinational logic)
```

```
        Q_next <= Q;
```

```
        Y      <= (others => '0');
```

```
        -- INSERT COMBINATIONAL BEHAVIOR HERE
```

```
        -- Q_next <= some_function_of(X, Q);
```

```
        -- Y      <= some_other_function_of(X, Q);
```

```
    end process;
```

```
    -- 2. SEQUENTIAL PROCESS:
```

```
    state_register : process(CLK)
```

```
    begin
```

```
        if rising_edge(CLK) then
```

```
            Q <= Q_next;
```

```
        end if;\
```

```
    end process;
```

```
end Behavioral;
```


Synchronous vs Asynchronous Circuits

- Asynchronous design is **more general** than synchronous design
 - the timing of the system is not limited by clocked registers
 - (just as analog circuits are more general than digital circuits)
- Synchronous circuits are **easier to design** than asynchronous circuits
 - (just as digital are easier than analog circuits)
- Despite decades of research on asynchronous circuits, virtually all digital systems are essentially synchronous
- Asynchronous circuits are **occasionally necessary** when communicating between **systems with different clocks** or when **receiving inputs at arbitrary times**
 - (just as analog circuits are necessary when communicating with the real world of continuous voltages)